


# Differential Equations

Alvin Lin

January 2018 - May 2018

## Circuits

Consider an RL series circuit:

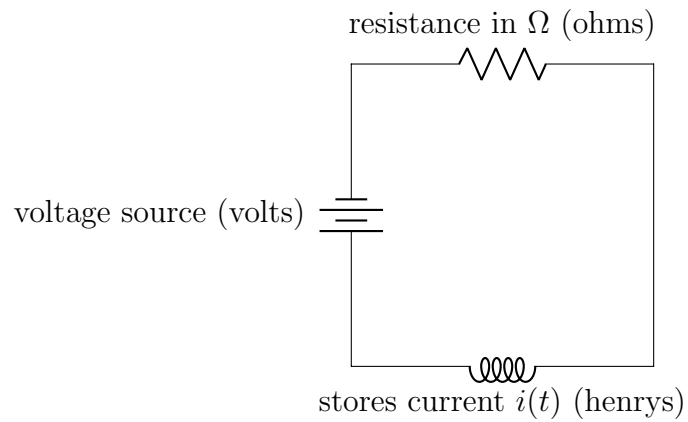

We want to find the current at time  $t$ . The current  $i$  is in amperes. According to **Kirchhoff's Law**, the sum of the the voltage drops across the inductor and the resistor is equal to the impressed voltage  $E(t)$ . The governing equation is:

$$L \frac{di}{dt} + Ri = E(t)$$

where  $E_L = L \frac{di}{dt}$  is the voltage drop across the inductor and  $Ri$  is the voltage drop across the resistor. This is a first order linear equation.

## Example

A 12-volt battery is connected to a series circuit where the inductance is  $\frac{1}{2}$ H and the resistance is  $10\Omega$ . Find the current at time  $t$  if the initial current is 0. Find the steady state current.

$$\begin{aligned}L \frac{di}{dt} + Ri &= E(t) \\ \frac{di}{dt} + \frac{R}{L}i &= \frac{E(t)}{L} \\ E &= 12V \quad L = \frac{1}{2} \quad R = 10\Omega \\ \frac{di}{dt} + \frac{10}{\frac{1}{2}}i &= \frac{12}{\frac{1}{2}} \\ \frac{di}{dt} + 20i &= 24 \\ \mu(t) &= e^{\int 20 dt} = e^{20t} \\ e^{20t} \frac{di}{dt} + 20ie^{20t} &= 24e^{20t} \\ \int \left( e^{20t} \frac{di}{dt} + 20ie^{20t} \right) dt &= \int 24e^{20t} dt \\ e^{20t}i &= \frac{24}{20}e^{20t} + c \\ i(t) &= \frac{6}{5} + ce^{-20t}\end{aligned}$$

Initially,  $i(0) = 0$ :

$$\begin{aligned}0 &= \frac{6}{5} + c \\ c &= -\frac{6}{5} \\ i(t) &= \frac{6}{5} - \frac{6}{5}e^{-20t} \\ \lim_{t \rightarrow \infty} \frac{6}{5} - \frac{6}{5}e^{-20t} &= \frac{6}{5}\end{aligned}$$

$\frac{6}{5}A$  is the steady state and  $-\frac{6}{5}e^{-20t}$  is the transient term.

## Example

An electromagnet is modeled as an RL circuit while it is being energized with a voltage source. If the inductance is 10H and the resistor is 30Ω, how long does it take a constant voltage to energize the electromagnet to 80% of its final value?

$$\begin{aligned}10 \frac{di}{dt} + 3i &= V \\ \frac{di}{dt} + \frac{3}{10}i &= \frac{V}{10} \\ \mu(t) &= e^{\int \frac{3}{10} dt} = e^{\frac{3}{10}t} \\ e^{\frac{3}{10}t} \frac{di}{dt} + \frac{3}{10} e^{\frac{3}{10}t} i &= \frac{1}{10} e^{\frac{3}{10}t} V \\ \int \left( e^{\frac{3}{10}t} \frac{di}{dt} + \frac{3}{10} e^{\frac{3}{10}t} i \right) dt &= \int \frac{1}{10} e^{\frac{3}{10}t} V dt \\ e^{\frac{3}{10}t} i &= \frac{1}{10} \frac{10}{3} e^{\frac{3}{10}t} + c \\ i &= \frac{V}{3} + ce^{-\frac{3}{10}t}\end{aligned}$$

Using  $i(0) = 0$ :

$$\begin{aligned}0 &= \frac{V}{3} + c \\ c &= -\frac{V}{3} \\ i(t) &= \frac{V}{3} - \frac{V}{3} e^{-\frac{3}{10}t} \\ 0.8 &= 1 - e^{-\frac{3}{10}t} \\ -0.2 &= -e^{-\frac{3}{10}t} \\ \ln(0.2) &= -\frac{3}{10}t \\ t &\approx 5.4\end{aligned}$$

You can find all my notes at <http://omgimanerd.tech/notes>. If you have any questions, comments, or concerns, please contact me at [alvin@omgimanerd.tech](mailto:alvin@omgimanerd.tech)