


Differential Equations

Alvin Lin

January 2018 - May 2018

Circuits

Consider an RL series circuit:

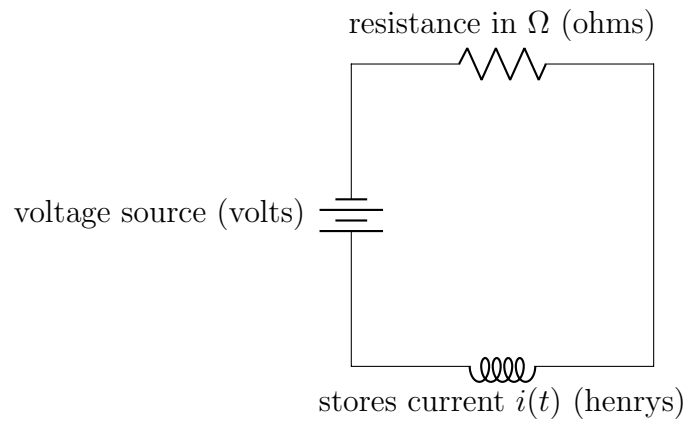

We want to find the current at time t . The current i is in amperes. According to **Kirchhoff's Law**, the sum of the the voltage drops across the inductor and the resistor is equal to the impressed voltage $E(t)$. The governing equation is:

$$L \frac{di}{dt} + Ri = E(t)$$

where $E_L = L \frac{di}{dt}$ is the voltage drop across the inductor and Ri is the voltage drop across the resistor. This is a first order linear equation.

Example

A 12-volt battery is connected to a series circuit where the inductance is $\frac{1}{2}$ H and the resistance is 10Ω . Find the current at time t if the initial current is 0. Find the steady state current.

$$L \frac{di}{dt} + Ri = E(t)$$
$$\frac{di}{dt} + \frac{R}{L}i = \frac{E(t)}{L}$$
$$E = 12V \quad L = \frac{1}{2} \quad R = 10\Omega$$

$$\frac{di}{dt} + \frac{10}{\frac{1}{2}}i = \frac{12}{\frac{1}{2}}$$

$$\frac{di}{dt} + 20i = 24$$

$$\mu(t) = e^{\int 20 dt} = e^{20t}$$

$$e^{20t} \frac{di}{dt} + 20ie^{20t} = 24e^{20t}$$

$$\int \left(e^{20t} \frac{di}{dt} + 20ie^{20t} \right) dt = \int 24e^{20t} dt$$

$$e^{20t}i = \frac{24}{20}e^{20t} + c$$

$$i(t) = \frac{6}{5} + ce^{-20t}$$

Initially, $i(0) = 0$:

$$0 = \frac{6}{5} + c$$

$$c = -\frac{6}{5}$$

$$i(t) = \frac{6}{5} - \frac{6}{5}e^{-20t}$$

$$\lim_{t \rightarrow \infty} \frac{6}{5} - \frac{6}{5}e^{-20t} = \frac{6}{5}$$

$\frac{6}{5}A$ is the steady state and $-\frac{6}{5}e^{-20t}$ is the transient term.

Example

An electromagnet is modeled as an RL circuit while it is being energized with a voltage source. If the inductance is 10H and the resistor is 30Ω, how long does it take a constant voltage to energize the electromagnet to 80% of its final value?

$$\begin{aligned}10 \frac{di}{dt} + 3i &= V \\ \frac{di}{dt} + \frac{3}{10}i &= \frac{V}{10} \\ \mu(t) &= e^{\int \frac{3}{10} dt} = e^{\frac{3}{10}t} \\ e^{\frac{3}{10}t} \frac{di}{dt} + \frac{3}{10} e^{\frac{3}{10}t} i &= \frac{1}{10} e^{\frac{3}{10}t} V \\ \int \left(e^{\frac{3}{10}t} \frac{di}{dt} + \frac{3}{10} e^{\frac{3}{10}t} i \right) dt &= \int \frac{1}{10} e^{\frac{3}{10}t} V dt \\ e^{\frac{3}{10}t} i &= \frac{1}{10} \frac{10}{3} e^{\frac{3}{10}t} + c \\ i &= \frac{V}{3} + ce^{-\frac{3}{10}t}\end{aligned}$$

Using $i(0) = 0$:

$$\begin{aligned}0 &= \frac{V}{3} + c \\ c &= -\frac{V}{3} \\ i(t) &= \frac{V}{3} - \frac{V}{3} e^{-\frac{3}{10}t} \\ 0.8 &= 1 - e^{-\frac{3}{10}t} \\ -0.2 &= -e^{-\frac{3}{10}t} \\ \ln(0.2) &= -\frac{3}{10}t \\ t &\approx 5.4\end{aligned}$$

You can find all my notes at <http://omgimanerd.tech/notes>. If you have any questions, comments, or concerns, please contact me at alvin@omgimanerd.tech