


# University Physics 2

Alvin Lin


January 2018 - May 2018
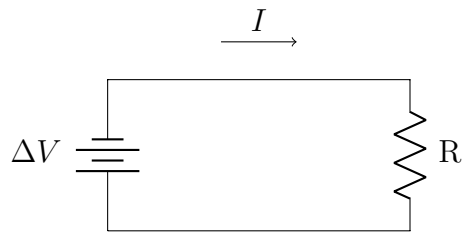
## Circuits

We will start with a microscopic pictures of current and resistance.



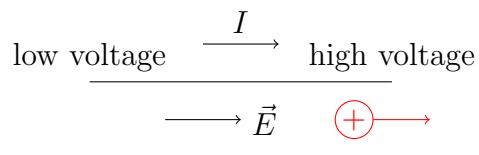Current will flow clockwise in this example, from the positive terminal of the battery through the wires, into the negative terminal. If we look at a small section of wire at the top.



We define current,  $I$  as the charge moved through the wire, per unit time.

$$I = \frac{dQ}{dt} = nqAV_d$$

Sometimes, we will want the current density:

$$J = \frac{I}{A} = nqV_d$$

All the constants can be defined and rewritten:


$$\rho = \frac{E}{J}$$

where  $\rho$  is the resistivity of the wire. It is a fundamental property of a material independent of area or density.

$$[\rho] = \frac{[E]}{[J]} = \frac{\frac{V}{m}}{\frac{A}{m^2}} = \frac{V \cdot m}{A}$$

$$\begin{aligned} E &= \rho J \\ EL &= \rho JL \\ \Delta V &= \frac{\rho IL}{A} \\ &= \frac{\rho L}{A} I \\ R &= \frac{\rho L}{A} \\ \Delta V &= IR \end{aligned}$$

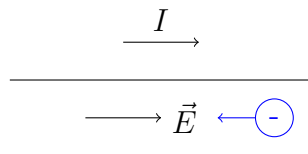This is known as Ohm's Law, where the units of resistance  $R$  are measured in ohms ( $\Omega$ ). All these derivations are done in terms of a positive charge, but in a wire, the charges that are moving are electrons.



## Temperature Dependence of Resistance

Resistivity depends on temperature:

$$(\rho - \rho_0) = \rho_0 \alpha (T - T_0)$$

where  $\rho$  is resistivity,  $T$  is temperature,  $\alpha$  is the temperature coefficient, and  $T_0, \rho_0$  are reference values. Note that this is similar to the equation of a line. Thus, the temperature coefficient can be determined by measuring these values and determining the slope of the line plotted by the resistivity at certain temperatures.

## Power

Power is energy per unit time. Recall that current is change in current over unit time.

$$I = \frac{\Delta Q}{\Delta t} \quad \Delta Q = I\Delta t$$

With potential energy:

$$\Delta U = \Delta QV$$

$$\Delta U = I\Delta tV$$



$$\frac{\Delta U}{\Delta t} = IV$$

$$P = IV$$

In relation to Ohm's Law:

$$P = IV = I^2R = \frac{V^2}{R}$$

## Equivalent Resistance (In Series)

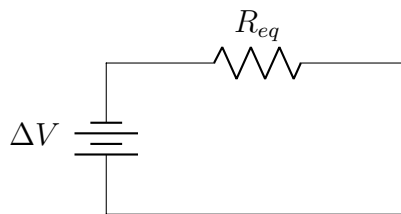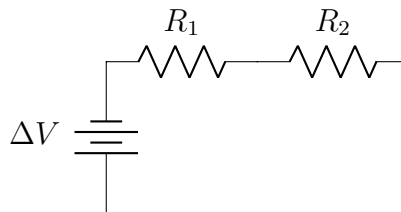

From conservation of charge:

$$I_1 = I_2 = I_{eq}$$

From conservation of energy and the equivalent circuit:

$$\Delta V = \Delta V_1 + \Delta V_2$$

From the equivalent circuit:

$$\begin{aligned}\Delta V &= IR_{eq} \\ \Delta V_1 + \Delta V_2 &= IR_{eq}\end{aligned}$$



Using Ohm's Law:

$$\begin{aligned}IR_1 + IR_2 &= IR_{eq} \\ R_1 + R_2 &= R_{eq}\end{aligned}$$

Compared to capacitance:

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

### Equivalent Resistance (In Parallel)

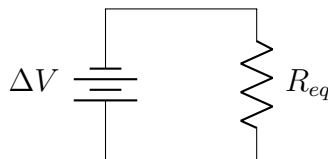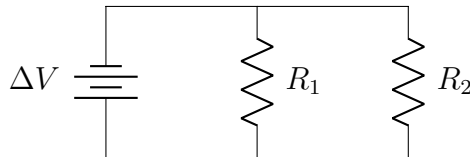

From conservation of energy:

$$\Delta V = \Delta V_1 = \Delta V_2$$

From conservation of charge:


$$I = I_1 + I_2$$

Using Ohm's Law:

$$\begin{aligned}\frac{\Delta V}{R_{eq}} &= \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2} \\ \frac{1}{R_{eq}} &= \frac{1}{R_1} + \frac{1}{R_2} \\ R_{eq} &= \frac{R_1 R_2}{R_1 + R_2}\end{aligned}$$

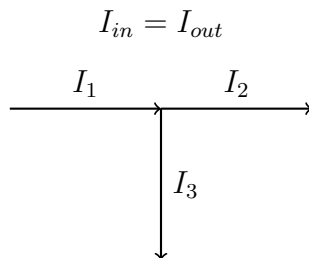
## Kirchhoff's Laws

At a junction or node, the current going in is equal to the current going out.



$$I_1 = I_2 + I_3$$

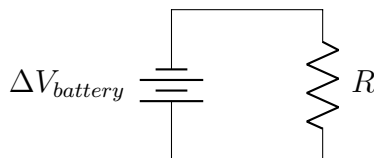This arises from the conservation of current/charge and is always true in a steady state. For a loop in a circuit, conservation of energy says:



$$\Delta V_{total} = 0$$

$$\Delta V_{battery} + \Delta V_{resistor} = 0$$

$$\Delta V_{battery} = -\Delta V_{resistor}$$


$$\Delta E = 0 = \Delta U = q\Delta V$$

The voltage drop is zero for a closed loop. The voltage drop across a resistor is negative if the loop chosen is in the same direction as the current. The voltage drop is positive if the opposite is true. For a battery, the voltage drop across it is positive if the loop goes from negative to positive.

### Solving Kirchhoff's Law Problems

1. Draw currents through each element. If you don't know the directions, guess.
2. Identify the number of loops and nodes.
3. Draw the chosen loops.
4. Write down one equation for each node and loop using Kirchhoff's Law.
5. Solve it as a system of equations.

### Example

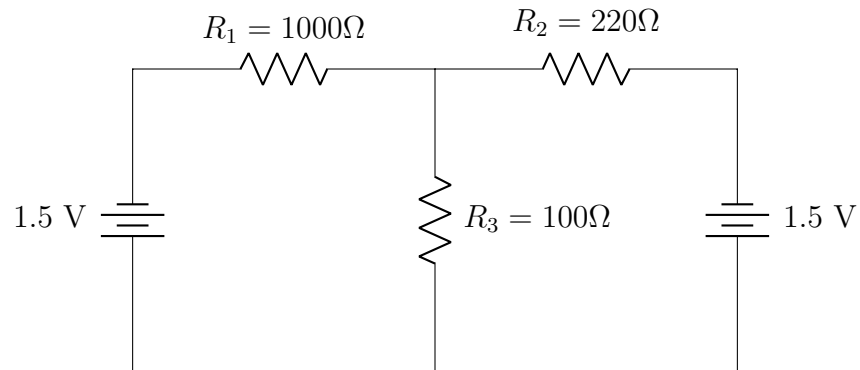

This yields a few equations. We will use these three to solve for the voltage drop:

$$1.5 - \Delta V_1 - \Delta V_3 = 0$$

$$1.5 - \Delta V_2 - \Delta V_3 = 0$$

$$I_1 + I_2 = I_3$$

We can substitute with Ohm's Law to yield a system of equations to solve for the voltage drops:

$$1.5 - \Delta V_1 - \Delta V_3 = 0$$

$$1.5 - \Delta V_2 - \Delta V_3 = 0$$


$$\frac{\Delta V_1}{R_1} + \frac{\Delta V_2}{R_2} = \frac{\Delta V_3}{R_3}$$

$$\Delta V_1 = \frac{55}{57}$$

$$\Delta V_2 = \frac{55}{57}$$

$$\Delta V_3 = \frac{61}{114}$$

### RC Circuits

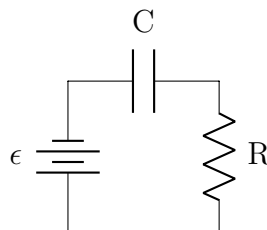

We can analyze this circuit using Kirchhoff's Law as well.

$$\begin{aligned}
 \epsilon - \Delta V_C - \Delta V_R &= 0 \\
 \epsilon - \frac{Q}{C} - IR &= 0 \\
 I &= \frac{dQ}{dt} \\
 I &= \frac{\epsilon}{R} - \frac{Q}{RC} \\
 \frac{d}{dt}I &= \frac{d}{dt} \left[ \frac{\epsilon}{R} - \frac{Q}{RC} \right] \\
 \frac{dI}{dt} &= 0 - \frac{1}{RC} \frac{dQ}{dt} \\
 \frac{dI}{dt} &= -\frac{1}{RC} I \\
 I(t) &= I_0 e^{-\frac{t}{RC}} \\
 I(t) &= \frac{\epsilon}{R} e^{-\frac{t}{RC}}
 \end{aligned}$$

This is the equation of the current through an RC circuit with an uncharged capacitor with  $\tau = RC$  as the time constant. We can also calculate the charge as it changes over time:

$$\begin{aligned}
 I &= \frac{dQ}{dt} \\
 \frac{dQ}{dt} &= \frac{\epsilon}{R} e^{-\frac{t}{RC}} \\
 Q(t) &= \int_0^t \frac{\epsilon}{R} e^{-\frac{t'}{RC}} dt' \\
 &= -\frac{\epsilon}{R} RC e^{-\frac{t}{RC}} + K \\
 Q(0) &= 0 \quad \therefore \quad K = \epsilon C \\
 Q(t) &= \epsilon C (1 - e^{-\frac{t}{RC}})
 \end{aligned}$$

When the capacitor is discharging:

$$\begin{aligned}\delta V_C &= \delta V_R \\ \frac{Q}{C} &= IR = -\frac{dQ}{dt}R \\ \frac{dQ}{Q} &= -\frac{1}{RC} dt \\ \int \frac{dQ}{Q} &= -\int \frac{1}{RC} dt \\ \ln\left(\frac{Q}{Q_0}\right) &= \frac{-t}{RC} \\ Q(t) &= Q_0 e^{\frac{-t}{RC}} \\ I(t) &= \frac{dQ}{dt} = \frac{-Q_0}{RC} e^{\frac{-t}{RC}}\end{aligned}$$

You can find all my notes at <http://omgimanerd.tech/notes>. If you have any questions, comments, or concerns, please contact me at [alvin@omgimanerd.tech](mailto:alvin@omgimanerd.tech)